

## ESM Lab Grading Report Template

Course Number: 5

Module: Lab 6 on PID Control

Lab Report Date \_\_\_\_12/13/2021\_\_\_\_

Student Name(s) \_\_Swapnil Ghonge and Harshwardhan Singh\_\_\_\_

***Each*** Section of this Lab Report Counts for 20 points. Points will be allocated as follows:

20 points: section fully meets requirements of this rubric

15 points: section mostly meets requirements of this rubric

10 points: section meets roughly half the requirements of this rubric

5 points: section does not meet requirements, but shows a weak attempt

0 points: section blank

**Goal:** The purpose of this lab is to learn how to construct a simple PID control system to control an LC oscillating circuit. We chose this system because it has the same 2<sup>nd</sup> order response as found in many control topologies such as robot arms, but our components are much more affordable. We will use our small DC motor from earlier labs as an inductor with resistor, and then add a 4.7 microfarad capacitor in series. All other components we will use are found inside the PSOC system.

**Background:** In a common motion control topology a microprocessor writes a number to a circuit, and circuit is designed to force the motor current to be proportional to that number. Because torque is proportional to current, the number is proportional to acceleration times rotary inertia ( $T = J \, dx^2/dt^2$ ). Acceleration of course, is the 2<sup>nd</sup> derivative of position, and velocity is the first derivative. Mathematically, the 2<sup>nd</sup> order equations for position control are identical to those of a series L-R-C circuit. This snippet from our schematic is for the L-R-C circuit.

In our circuit the input and control will come from a DAC\_1, per this snippet below of the schematic.

The system output be the voltage across the capacitor, as shown in this snippet of the schematic, and per the red color on our scope traces.

We will use the successive approximation (ADC SAR ADC) set to its fastest conversion speed to minimize the phase delay. Software reads the voltage from the capacitor, and calculates the proportional, derivative and integral terms, adds a feedforward term, and outputs that number to DAC\_1. We will test our circuit by measuring the response of our system to a step input.

We will use all four of the PSoC high current op amps in parallel to get enough current to run this circuit.

We will show you how to tune a PID system to get a good step response, as well as how to write the code to prevent saturation and overload. We will use scope traces and our USB UART built into PSoC to send data to the Teraterm program on your PC. There is a detailed explanation in the video for how to write the code. It is important that you watch the whole video to give you guidance in code writing.

(A) Functional demonstration of your circuit to our TA. In this exercise, you schedule an appointment with your TA to show that your hardware functions as designed. For the Closed Loop C Motor Control lab, this will involve the following steps:

1. Show that all hardware is in place, and that your PSoC software can control the motor current.
2. Show the scope traces of your current flow, along with the desired current setting from the DAC.


If you are an on-campus student, then show your circuit to one of our TA's during office hours.

If you are a distance learning student, make an online appointment with your TA to demonstrate your work via Zoom meeting or other Web-based meeting tool. You can use the camera on your laptop PC or suitable plug-in webcam (Logitech etc.) to demonstrate a working circuit.

(B) Place photos here of your hardware setup, including PSoC board, connections to Oscilloscope or nScope, wiring, LCD Display, components, etc.

Label all components.

Sample photo is shown here. (Make sure to delete the sample and place your own photos here).

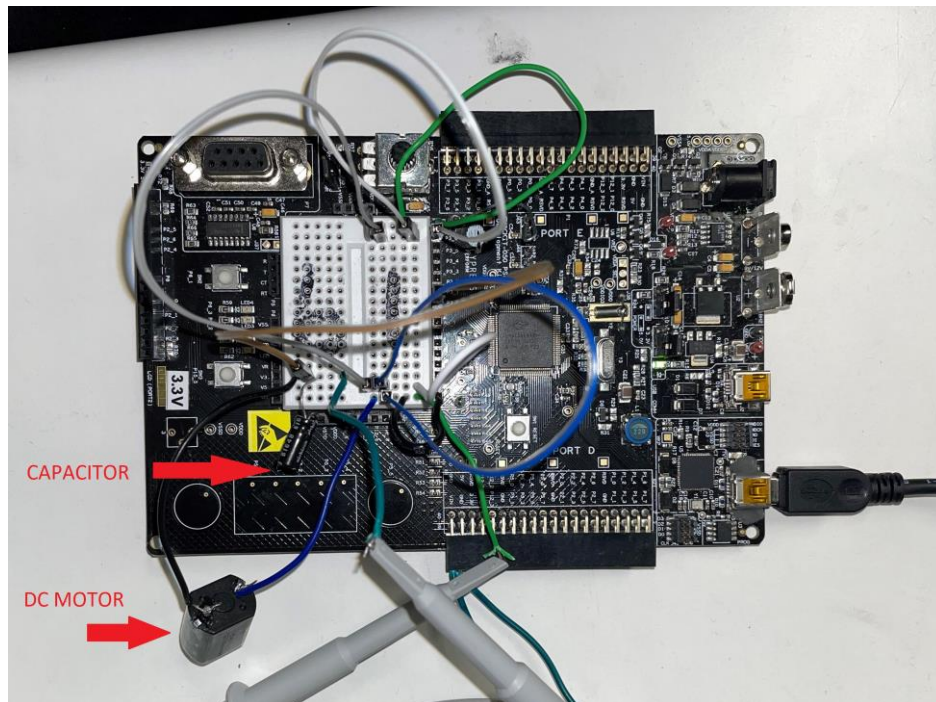

*Figure 1: Hardware Setup with labelling of capacitor and DC motor*

(C) Place complete PSoC schematic here. This schematic must include internal components from the PSoC board (amplifier, ADC, etc.), as well as external components (power diode, motor, n-channel power FET, etc.).



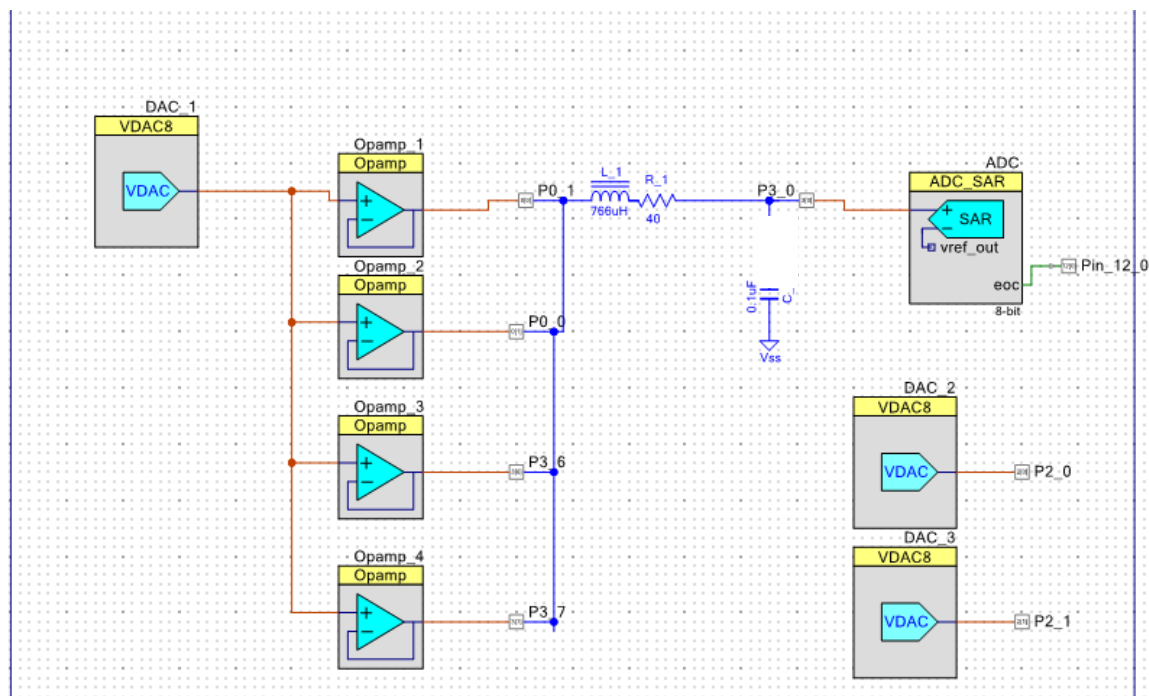
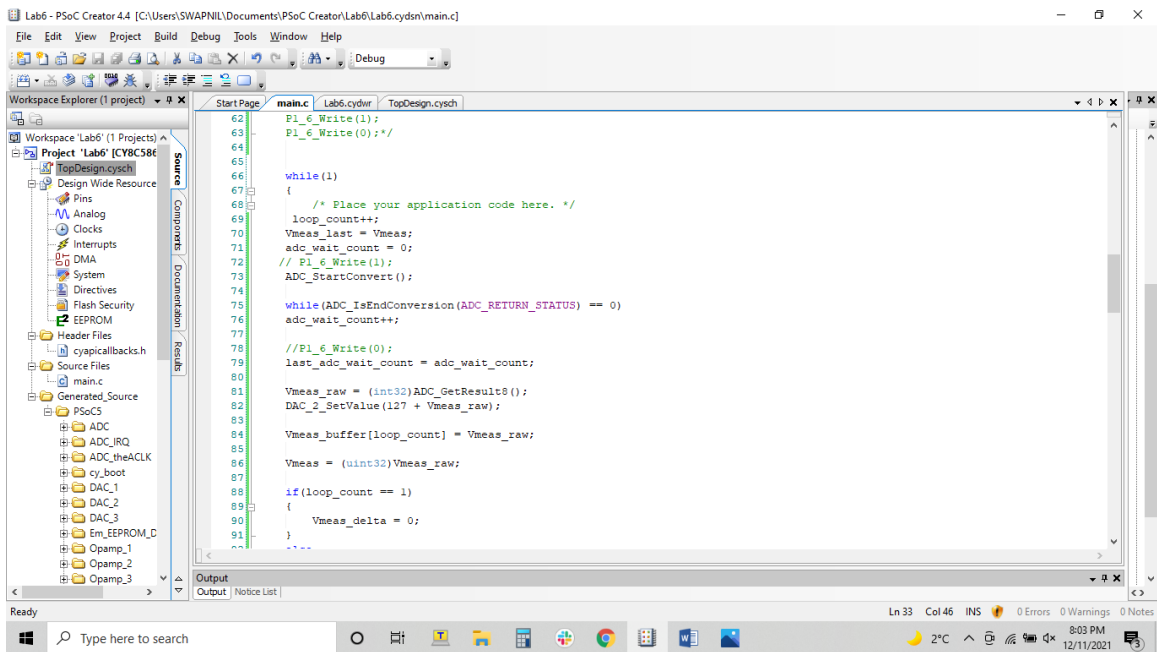
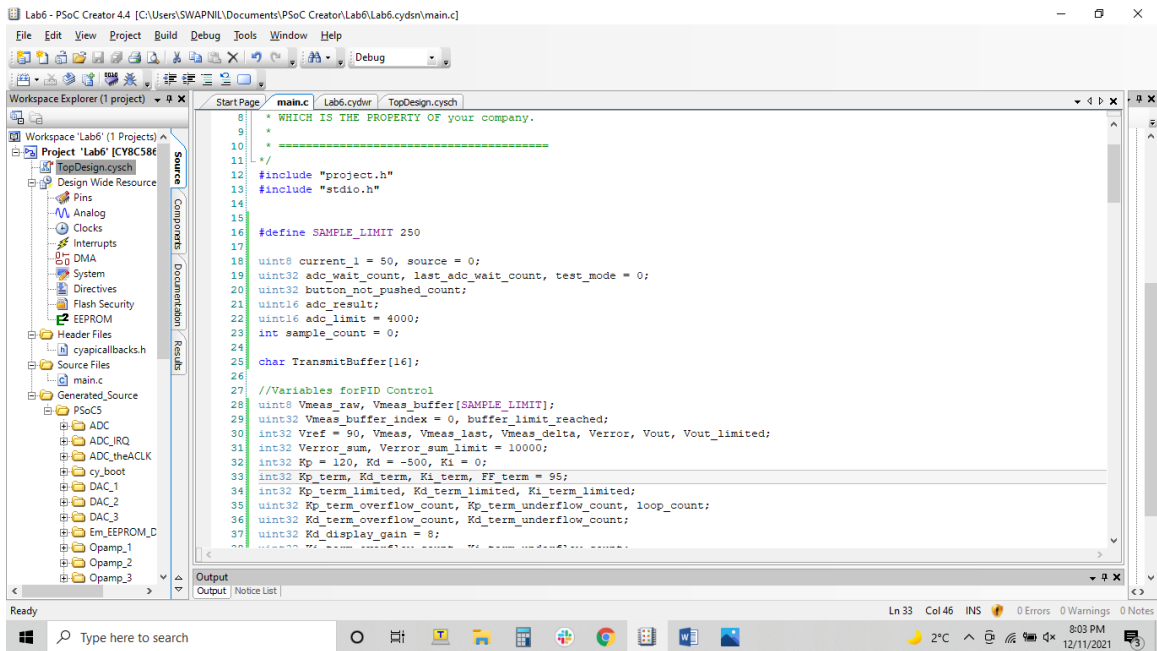




Figure 2: Hardware PSoC Schematic

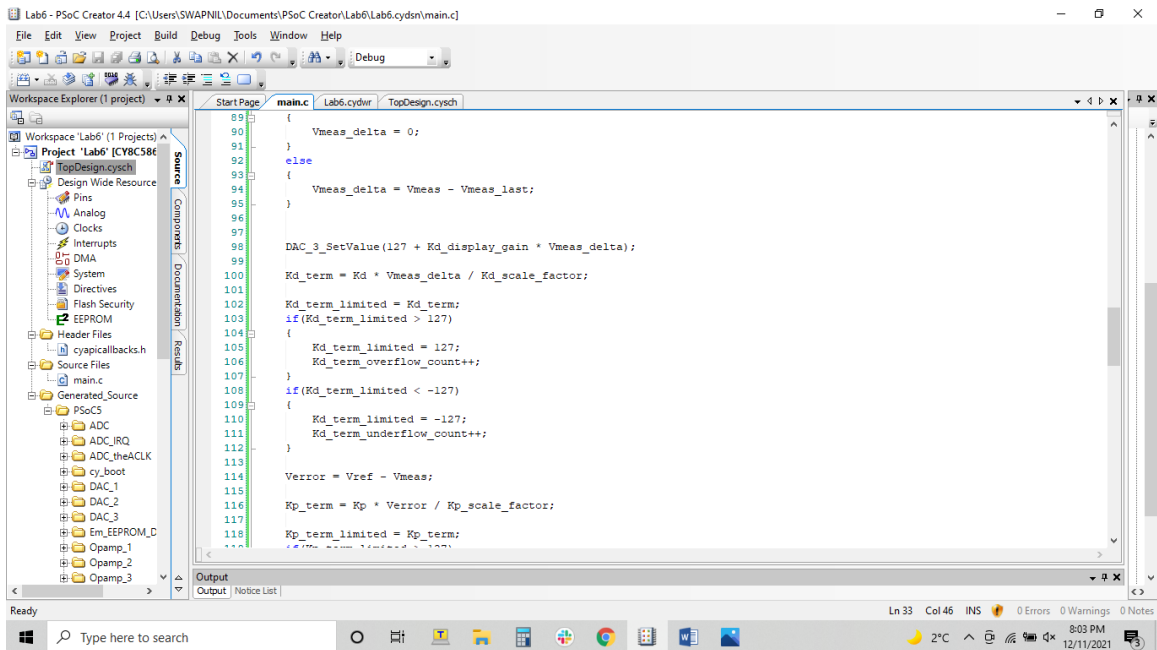
(D) Complete PSoC software. This software must include calls to all internal functions, appropriate comments, and functional code that you included. We will not grade you on the exact syntax and structure, as there are numerous ways to structure the code and still provide the temperature measurement function. Instead, we will grade you on the completeness of the code relative to using the appropriate PSoC functions to gather the necessary data.

Along with this completed file, upload to Canvas a .zip file with the PSoC file main.c. This screen shot from PSoC shows where the file main.c is located in your main screen.



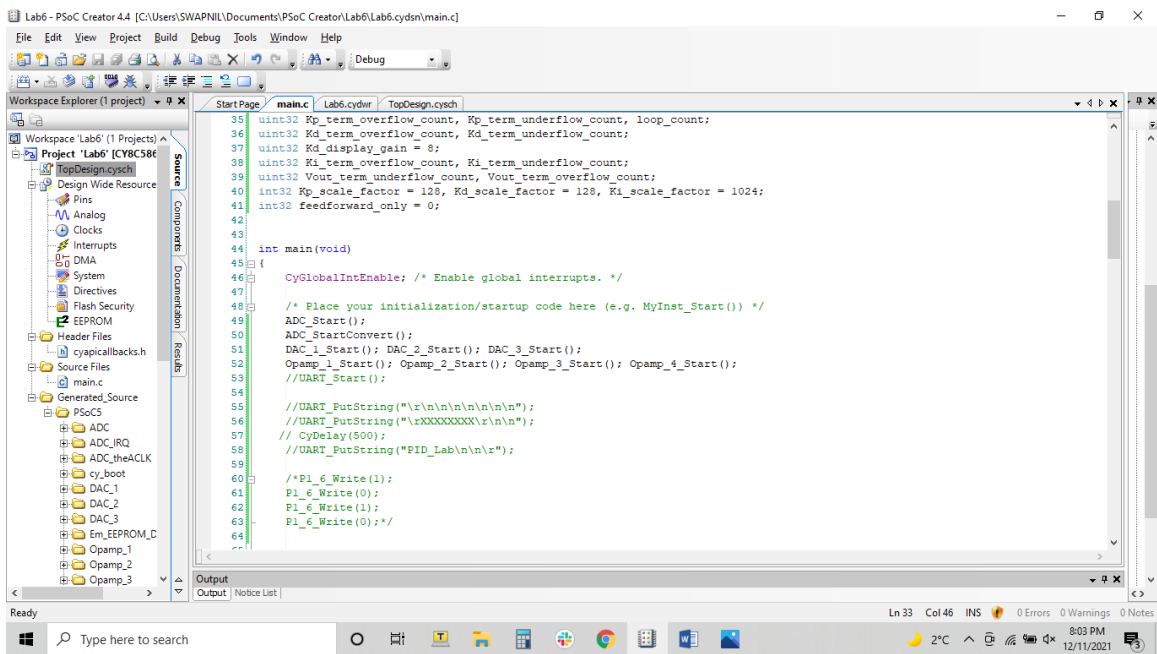

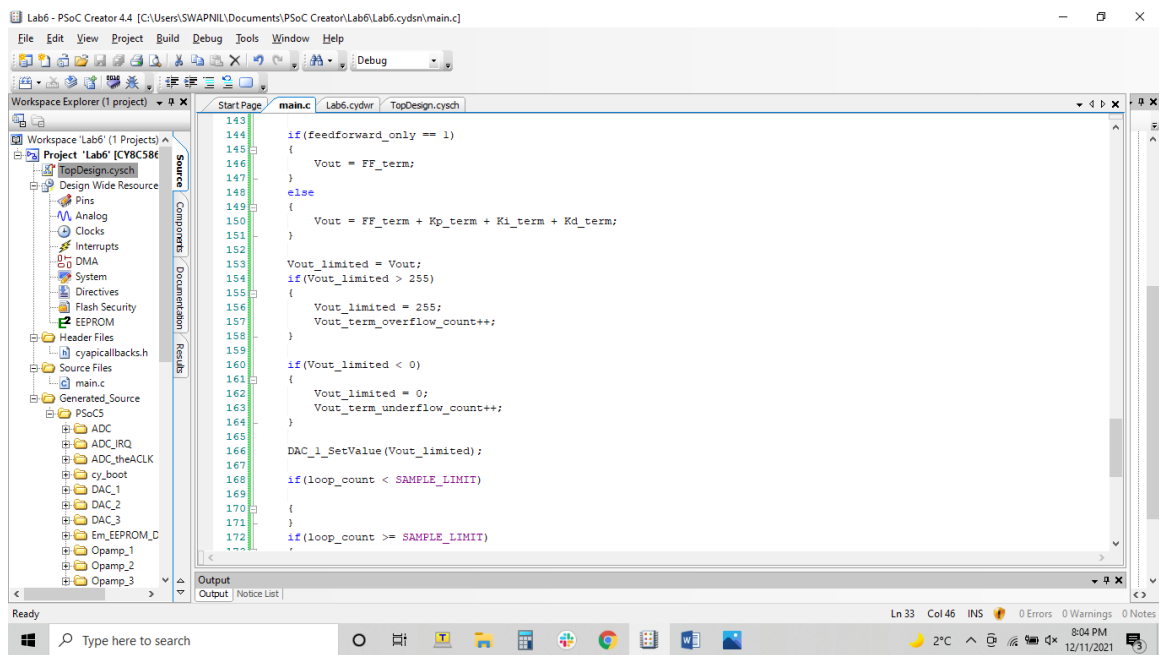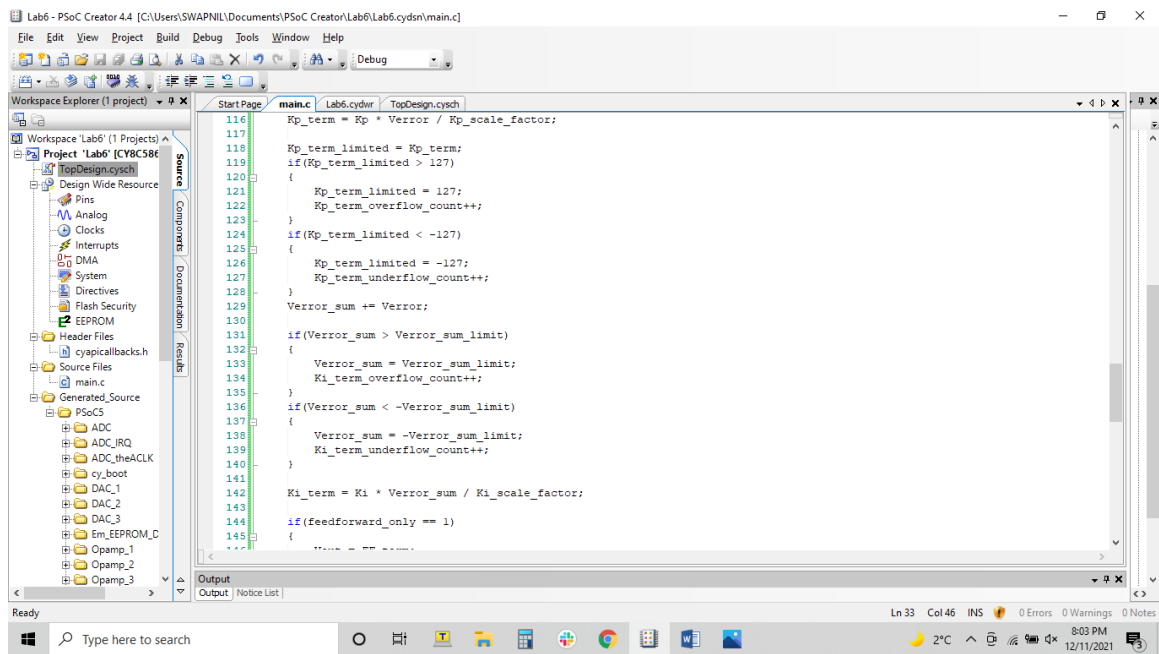

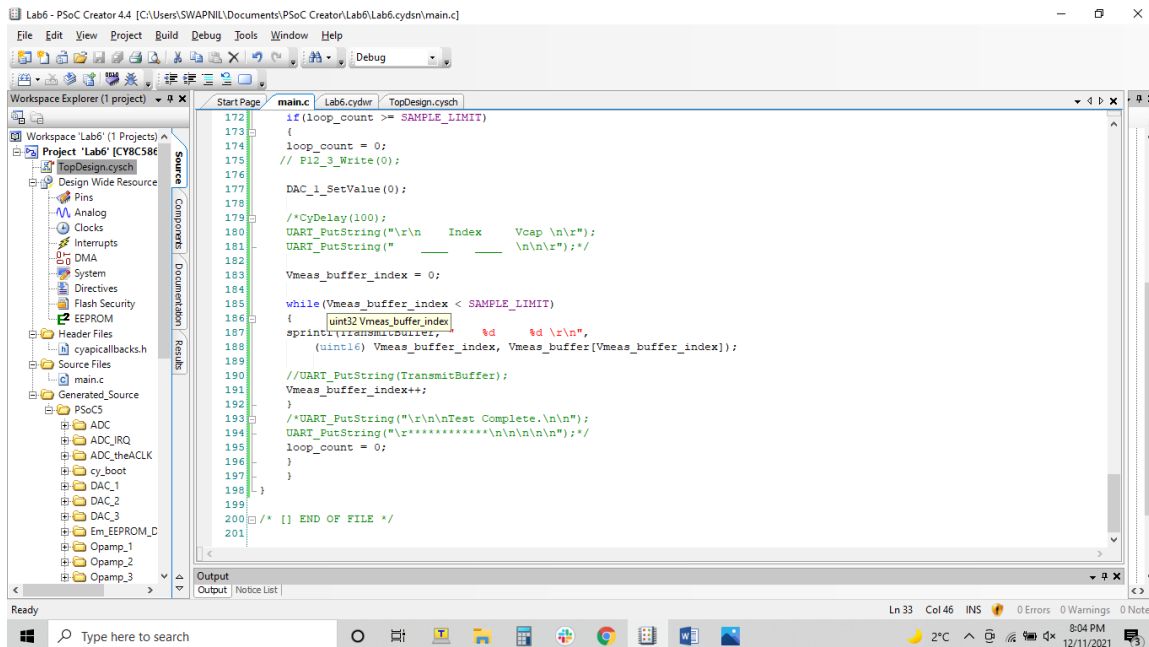

E) Place screenshots from your oscilloscope or nScope showing the output, the voltage of the capacitor, and the input DAC\_1.

Vary your values for Kp, Ki, Kd, and FF\_term to get  $V_{ref} = 120 \pm 1$ , a stable input value for DAC\_1, and no more than 1.5 oscillations of the output before it settles at its final value. Use your Teraterm program to view Vref.

You will not get the exact values shown in our video because your motor inductance and resistance, as well as the exact value of your 4.7 microfarad capacitor will vary from what we used in our system. Your PSoC board may have varying resistances. Your code will likely execute at a different clock cycle than ours, as your goal is to make it *functionally* equivalent, *not* the same line by line. So, you will need to do your own experiment to optimize the values.

Sample screenshots are shown here. (Make sure to delete the sample and place your own screen shots here).

Note: The yellow dotted trace below is for Vref.



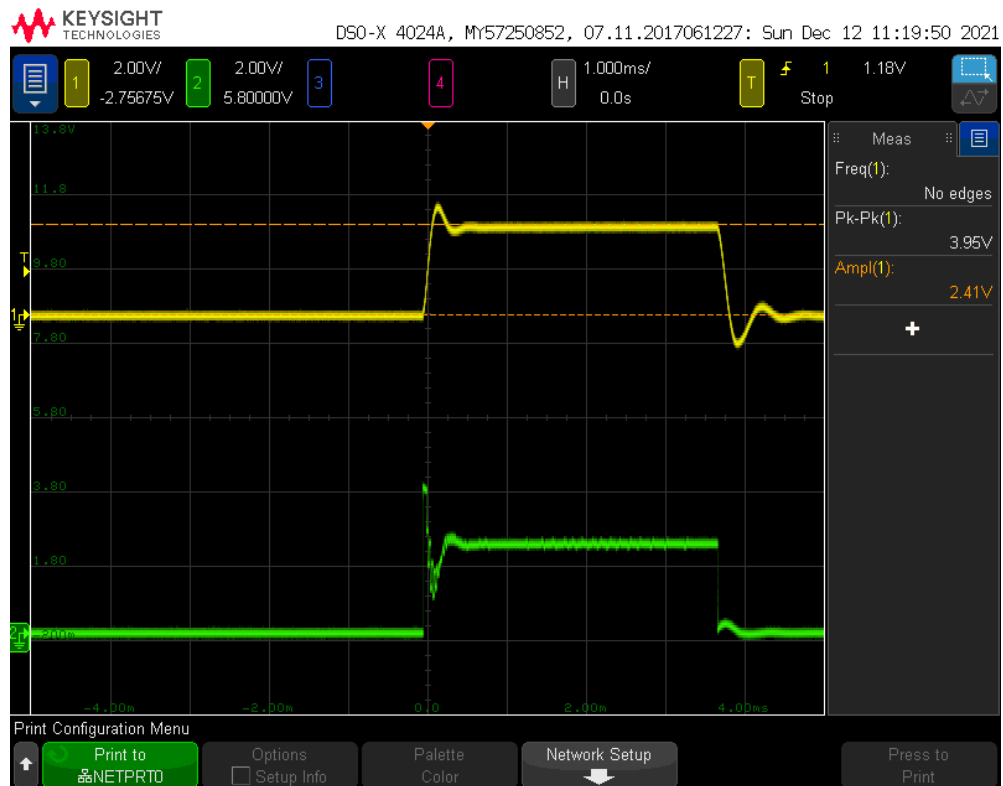


Figure 4: Oscilloscope,  $V_{ref} = 90$ ,  $K_P = 120$ ,  $K_D = -500$ ,  $K_i = 0$  and  $FF_{term} = 190$

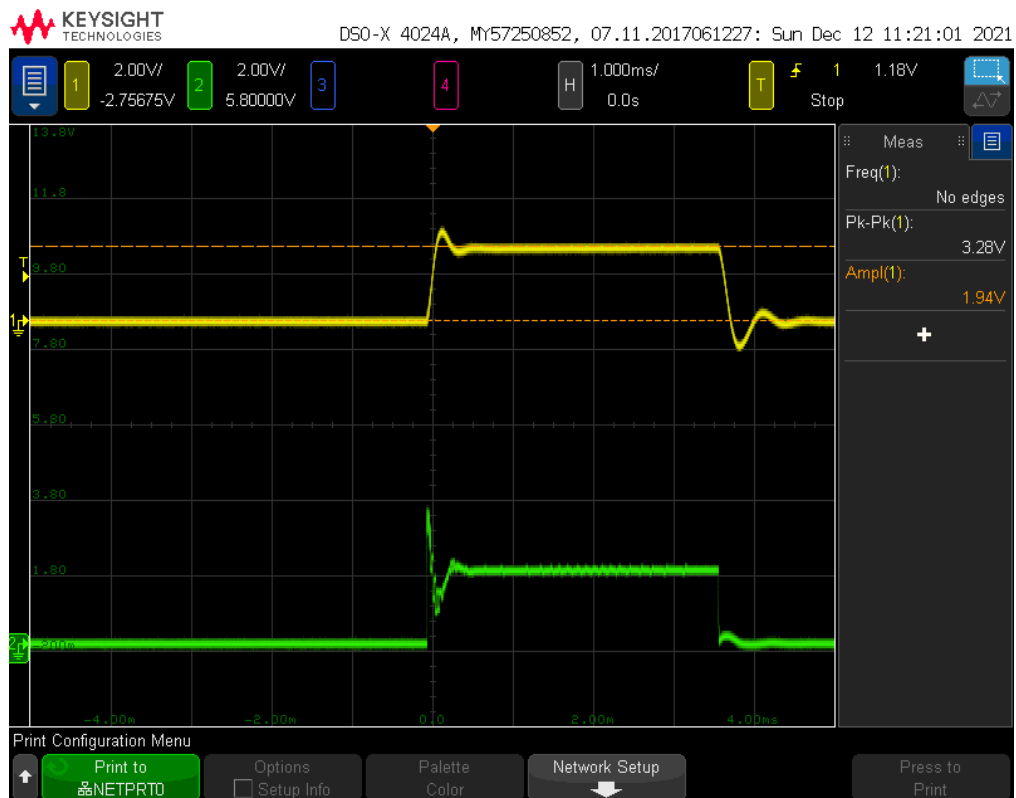


Figure 3: Oscilloscope,  $V_{ref} = 110$ ,  $K_P = 120$ ,  $K_D = -500$ ,  $K_i = 0$  and  $FF_{term} = 120$

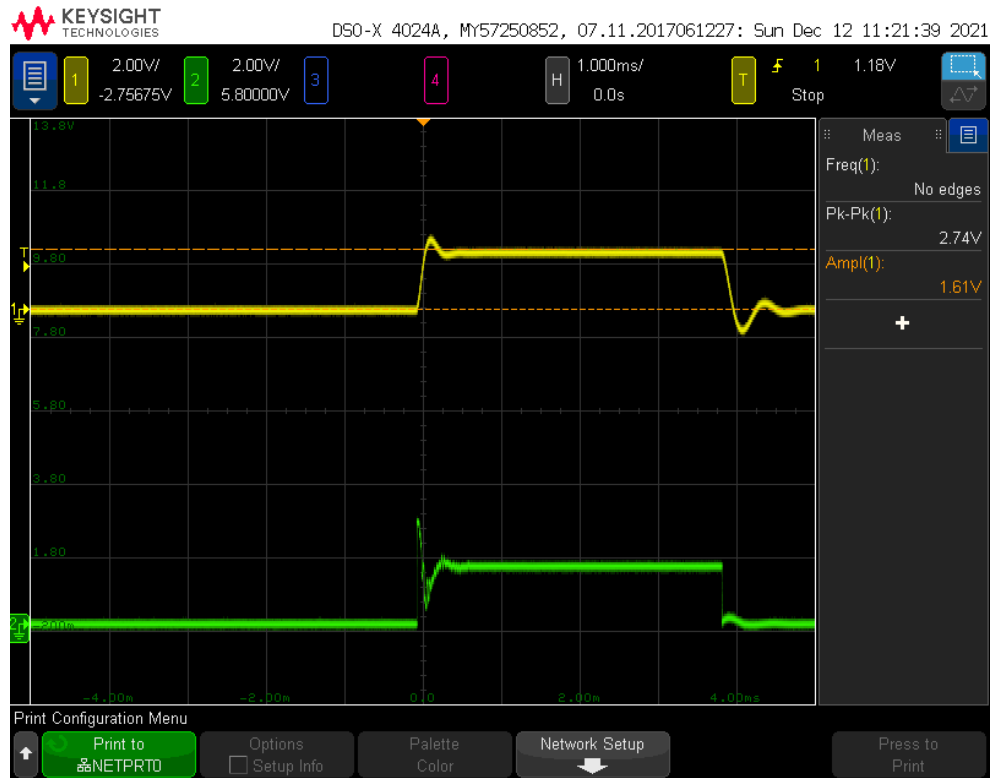


Figure 5: Oscilloscope,  $V_{ref} = 90$ ,  $K_P = 120$ ,  $K_D = -500$ ,  $K_i = 0$  and  $FF_{term} = 95$

|     | $V_{REF}$ | $K_P$ | $K_D$ | $K_i$ | $FF_{term}$ | Desired | Actual |
|-----|-----------|-------|-------|-------|-------------|---------|--------|
| 100 | 90        | 120   | -500  | 0     | 95          | 1.60    | 1.61   |
| 120 | 110       | 120   | -500  | 0     | 120         | 1.92    | 1.94   |
| 150 | 90        | 120   | -500  | 0     | 190         | 2.40    | 2.41   |